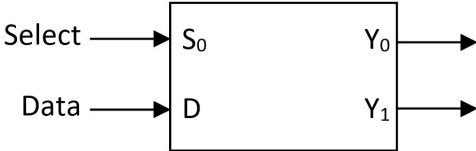
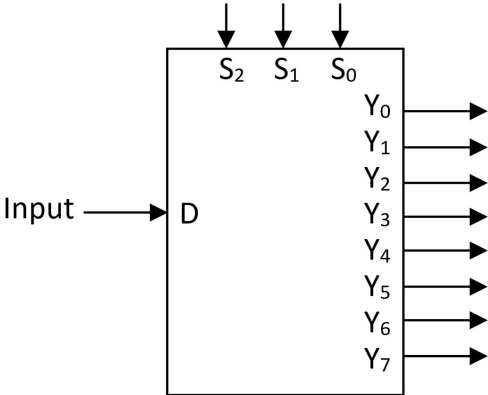


Episode 6.10 - Demultiplexers


(Transcript URL: <https://intertainment.com/episode-6-10-demultiplexers/>)

Show Description: A demultiplexer takes a single data stream and routes it to a selected output channel, a bit like one of those old A-B printer switches we used to physically select which printer we were sending data to. In this episode, we show how to design one.

Podcast Timestamp	Supporting Details																																																																																													
2:08	<div><p>Block Diagram of a One-to-Two Demultiplexer</p></div>																																																																																													
3:28	<div><p>Truth Table for an Active-High One-to-Four Demultiplexer</p><table><tr><th>S₁</th><th>S₀</th><th>D</th><th>Y₀</th><th>Y₁</th><th>Y₂</th><th>Y₃</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td><td>1</td></tr></table><p>or</p><table><tr><th>S₀</th><th>S₁</th><th>Y₀</th><th>Y₁</th><th>Y₂</th><th>Y₃</th></tr><tr><td>0</td><td>0</td><td>D</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>D</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td><td>D</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td><td>D</td></tr></table></div>	S ₁	S ₀	D	Y ₀	Y ₁	Y ₂	Y ₃	0	0	0	0	0	0	0	0	0	1	1	0	0	0	0	1	0	0	0	0	0	0	1	1	0	1	0	0	1	0	0	0	0	0	0	1	0	1	0	0	1	0	1	1	0	0	0	0	0	1	1	1	0	0	0	1	S ₀	S ₁	Y ₀	Y ₁	Y ₂	Y ₃	0	0	D	0	0	0	0	1	0	D	0	0	1	0	0	0	D	0	1	1	0	0	0	D
S ₁	S ₀	D	Y ₀	Y ₁	Y ₂	Y ₃																																																																																								
0	0	0	0	0	0	0																																																																																								
0	0	1	1	0	0	0																																																																																								
0	1	0	0	0	0	0																																																																																								
0	1	1	0	1	0	0																																																																																								
1	0	0	0	0	0	0																																																																																								
1	0	1	0	0	1	0																																																																																								
1	1	0	0	0	0	0																																																																																								
1	1	1	0	0	0	1																																																																																								
S ₀	S ₁	Y ₀	Y ₁	Y ₂	Y ₃																																																																																									
0	0	D	0	0	0																																																																																									
0	1	0	D	0	0																																																																																									
1	0	0	0	D	0																																																																																									
1	1	0	0	0	D																																																																																									
5:44	<div><p>Block Diagram of a One-to-Eight Demultiplexer</p></div>																																																																																													

Podcast Timestamp	Supporting Details
5:58	<p>Complete Boolean Logic for an Active-High One-to-Four Demultiplexer</p> <p>Complete Boolean Logic for an Active-High One-to-Four Demultiplexer</p>
9:13	<p>Complete Boolean Logic for an Active-Low One-to-Four Demultiplexer</p> <p>Complete Boolean Logic for an Active-Low One-to-Four Demultiplexer</p>

5:58

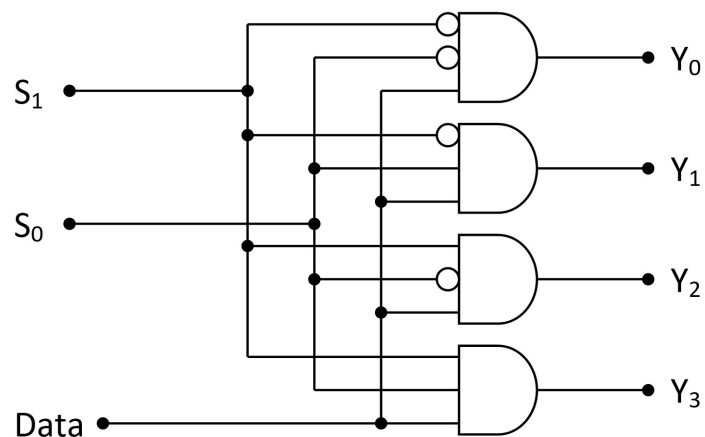Complete Boolean Logic for an Active-High One-to-Four Demultiplexer

9:13

Complete Boolean Logic for an Active-Low One-to-Four Demultiplexer